

Experiment No. 7

Utilization of on-board resources of BASYS-3 FPGA Kit

OBJECTIVE: To realize digital logic through Verilog programs targeting the on-board peripherals of Basys-3 FPGA kit.

THEORY: The Basys-3 FPGA board has the following features:

- 1,800 Kbits of fast block RAM
- 33,280 logic cells in 5200 slices (each slice contains four 6-input LUTs and 8 flip-flops)
- Five clock management tiles, each with a phase-locked loop (PLL)
- 90 DSP slices
- Internal clock speeds exceeding 450MHz
- On-chip analog-to-digital converter (XADC)
- 16 user switches
- 16 user LEDs
- 5 user pushbuttons
- 4-digit 7-segment display
- Three Pmod connectors
- Pmod for XADC signals
- 12-bit VGA output
- USB-UART bridge
- Serial Flash
- Digilent USB-JTAG port for FPGA programming and communication
- USB HID Host for mice, keyboards and memory sticks

EXAMPLE 7.1: Write a sequential Verilog code for an 8-bit ALU, verify the design by simulation, and then implement it on the Basys-3 FPGA kit.

Solution:

Truth Table of 8-bit ALU

Input A	Input B	Select lines ALU_Sel	Operation	Output ALU_Out	CarryOut
00000011	00000011	000	Addition	00000110	0
00000011	00000011	001	Subtraction	00000000	0
00000011	00000011	010	Multiplication	00001001	0
00000011	00000011	011	Division	00000001	0
00000011	00000011	100	Logical left shift of A	00000110	0
00000011	00000011	101	Logical right shift of A	00000001	0
00000011	00000011	110	Rotate left of A	00000110	0
00000011	00000011	111	Rotate right of A	10000001	0

Verilog Code:

```
module ALU( input [7:0] A,B,                // ALU 8-bit Inputs
            input [2:0] ALU_Sel,           // ALU Selection
            output [7:0] ALU_Out,          // ALU 8-bit Output
            output CarryOut);              // Carry Out Flag
    reg [7:0] ALU_Result;
    wire [8:0] tmp;
    assign ALU_Out = ALU_Result;
    assign tmp = {1'b0,A} + {1'b0,B};
    assign CarryOut = tmp[8];
    always @(*)
    begin
        case(ALU_Sel)
            4'b000: // Addition
                ALU_Result = A + B ;
            4'b001: // Subtraction
                ALU_Result = A - B ;
            4'b010: // Multiplication
                ALU_Result = A * B;
            4'b011: // Division
                ALU_Result = A/B;
            4'b100: // Logical shift left
                ALU_Result = A<<1;
            4'b101: // Logical shift right
                ALU_Result = A>>1;
            4'b110: // Rotate left
                ALU_Result = {A[6:0],A[7]};
            4'b111: // Rotate right
                ALU_Result = {A[0],A[7:1]};
            default: ALU_Result = A + B ;
        endcase
    end
endmodule
```

Simulation Results:

Input: A [7:0] = 0000 0011, B [7:0] = 0000 0011, ALU_Sel[2:0]=010

Output: ALU_Out[7:0] = 0000 0001, CarryOut=0

 


Fig. 7.1: Simulation results of example 7.1

IO Pin Assignment:

Bit	Input A	Input B	ALU_Sel	Output ALU_Out	CarryOut
0	V17	V2	T17	V13	U16
1	V16	T3	U18	V3	
2	W16	T2	W19	W3	
3	W17	R3		U3	
4	W15	W2		P3	
5	V15	U1		N3	
6	W14	T1		P1	
7	W13	R2		L1	

Hardware Results:

Input: A[7:0]

SW7	SW6	SW5	SW4	SW3	SW2	SW1	SW0
OFF	OFF	OFF	OFF	OFF	OFF	ON	ON

Input: B[7:0]

SW15	SW14	SW13	SW12	SW11	SW10	SW9	SW8
OFF	OFF	OFF	OFF	OFF	OFF	ON	ON

Input: ALU_Sel[2:0]

BTNL	BTNC	BTNR
ON	OFF	ON

Output: ALU_Out[7:0]



LD15	LD14	LD13	LD12	LD11	LD10	LD9	LD8
OFF	OFF	OFF	OFF	OFF	OFF	OFF	ON

Output: CarryOut

LD0
OFF

EXAMPLE 7.2: Write a Verilog code to display the hexadecimal equivalent of the 16-bit binary input, given through the user switches, on the seven-segment display of the Basys-3 FPGA kit.

Solution:

 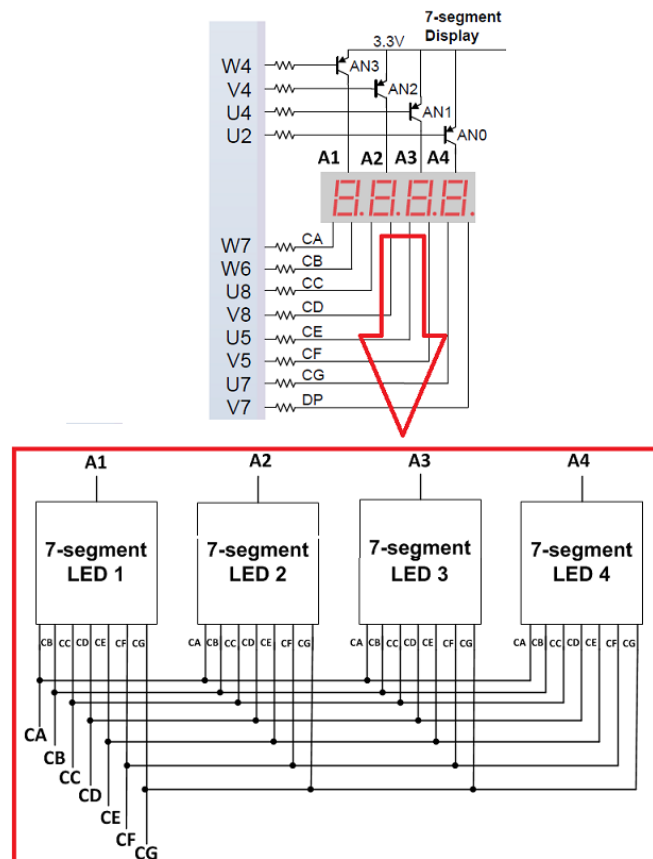

Verilog Code:

```
module Seven_segment(
    input clock_100Mhz, // 100 Mhz clock source on Basys 3 FPGA
    input reset, // Reset
    input [15:0] switch, // Binary input
    output reg [3:0] Anode_Activate, // anode signals of 7-segment LED display
    output reg [6:0] LED_out // cathode patterns of the 7-segment LED display
);

reg [3:0] LED_BCD;
reg [19:0] refresh_counter;
wire [1:0] Digit_activator;

always @(posedge clock_100Mhz or posedge reset)
begin
    if(reset==1)
        refresh_counter <= 0;
    else
        refresh_counter <= refresh_counter + 1;
end

assign Digit_activator = refresh_counter[19:18];

always @(*)
begin
    case(Digit_activator)
        2'b00: begin
            Anode_Activate = 4'b0111;
            // activate display1 and deactivate display2, 3, 4
            LED_BCD = switch[15:12];
            // the first digit of the 16-bit number
        end
        2'b01: begin
            Anode_Activate = 4'b1011;
            // activate display2 and deactivate display1, 3, 4
            LED_BCD = switch[11:8];
            // the second digit of the 16-bit number
        end
        2'b10: begin
            Anode_Activate = 4'b1101;
            // activate display 3 and deactivate display2, 1, 4
            LED_BCD = switch[7:4];
            // the third digit of the 16-bit number
        end
    end
```

```

        2'b11: begin
            Anode_Activate = 4'b1110;
            // activate LED4 and Deactivate LED2, LED3, LED1
            LED_BCD = switch[3:0]; // the fourth digit of the 16-bit number
        end
    endcase
end
// Cathode patterns of the 7-segment LED display
always @(*)
begin
    case(LED_BCD)
        4'b0000: LED_out = 7'b0000001; // "0"
        4'b0001: LED_out = 7'b1001111; // "1"
        4'b0010: LED_out = 7'b0010010; // "2"
        4'b0011: LED_out = 7'b0000110; // "3"
        4'b0100: LED_out = 7'b1001100; // "4"
        4'b0101: LED_out = 7'b0100100; // "5"
        4'b0110: LED_out = 7'b0100000; // "6"
        4'b0111: LED_out = 7'b0001111; // "7"
        4'b1000: LED_out = 7'b0000000; // "8"
        4'b1001: LED_out = 7'b0000100; // "9"
        4'b1010: LED_out = 7'b0001000; // "A"
        4'b1011: LED_out = 7'b1100000; // "b"
        4'b1100: LED_out = 7'b0110001; // "C"
        4'b1101: LED_out = 7'b1000010; // "d"
        4'b1110: LED_out = 7'b0110000; // "E"
        4'b1111: LED_out = 7'b0111000; // "F"
        default: LED_out = 7'b1111111;
    endcase
end
endmodule

```

Simulation Results:

Input: switch[15:0] = 0100 0101 0110 0011, reset = 1→0, clock=100MHz

Output:

Clock_pulses	Digit_activator	LED_BCD	LED_out (7-segment code)
at 1 st pulse	0 (1 st 7-seg display)	4	1001100
at (1x2 ¹⁸) th pulse	1 (2 nd 7-seg display)	5	0100100
at (2x2 ¹⁸) th pulse	2 (3 rd 7-seg display)	6	0100000
at (3x2 ¹⁸) th pulse	3 (4 th 7-seg display)	3	0000110

The above sequence keeps repeating at an interval of 2¹⁸ clock pulses

 


Fig. 7.2: Simulation results of example 7.2

Hardware Results:

Input: switch[15:0]

SW 15	SW 14	SW 13	SW 12	SW 11	SW 10	SW 9	SW 8	SW 7	SW 6	SW 5	SW 4	SW 3	SW 2	SW 1	SW 0
OFF	ON	OFF	OFF	OFF	ON	OFF	ON	OFF	ON	ON	OFF	OFF	OFF	ON	ON

Output:



EXAMPLE 7.3: Write a Verilog code to display the decimal equivalent of the 4-bit binary number, input through the user switches, on the seven-segment display of the Basys 3 kit.

Solution:

Binary Input	Decimal digit - 1	Decimal digit - 0
0000	0	0
0001	0	1
0010	0	2
0011	0	3
0100	0	4
0101	0	5
0110	0	6
0111	0	7
1000	0	8
1001	0	9
1010	1	0
1011	1	1
1100	1	2
1101	1	3
1110	1	4
1111	1	5

Verilog Code:

```
module Bin_2_Dec(
    input clock_100Mhz, // 100 Mhz clock source on Basys 3 FPGA
    input reset, // reset
    input [3:0] switch, //4-bit Binary input
    output reg [3:0] Anode_Activate,
                                     // anode signals of the 7-segment LED display
    output reg [6:0] LED_out // cathode patterns of the 7-segment LED display
);

reg Z;
reg [3:0] LED_BCD;
reg [19:0] refresh_counter;
wire [1:0] Digit_activator;

always @(posedge clock_100Mhz or posedge reset)
begin
    if(reset==1)
        refresh_counter <= 0;
    else
        refresh_counter <= refresh_counter + 1;
end

assign Digit_activator = refresh_counter[18];

always @(*)
begin
    Z = (switch>4'b1001)?1:0;
    case(Digit_activator)
    2'b0: begin
        Anode_Activate = 4'b1101;
        LED_BCD = {3'b000,Z};
    end
    2'b1: begin
        Anode_Activate = 4'b1110;
        if(Z==1)
            LED_BCD = switch-4'b1010;
        else
            LED_BCD = switch;
        end
    endcase
end
```



```
// Cathode patterns of the 7-segment LED display
always @(*)
begin
    case(LED_BCD)
        4'b0000: LED_out = 7'b0000001; // "0"
        4'b0001: LED_out = 7'b1001111; // "1"
        4'b0010: LED_out = 7'b0010010; // "2"
        4'b0011: LED_out = 7'b0000110; // "3"
        4'b0100: LED_out = 7'b1001100; // "4"
        4'b0101: LED_out = 7'b0100100; // "5"
        4'b0110: LED_out = 7'b0100000; // "6"
        4'b0111: LED_out = 7'b0001111; // "7"
        4'b1000: LED_out = 7'b0000000; // "8"
        4'b1001: LED_out = 7'b0000100; // "9"
        default: LED_out = 7'b1111111; // "0"
    endcase
end
endmodule
```

Simulation Results:

Input: switch[3:0]=1100, reset = 1→0, clock=100MHz

Output:

Clock_pulses	Digit_activator	LED_BCD	LED_out (7-segment code)
at 1 st pulse	0 (3 rd 7-seg display)	1	1001111
at (1x2 ¹⁸) th pulse	1 (4 th 7-seg display)	2	0010010

The above sequence keeps repeating at an interval of 2¹⁸ clock pulses

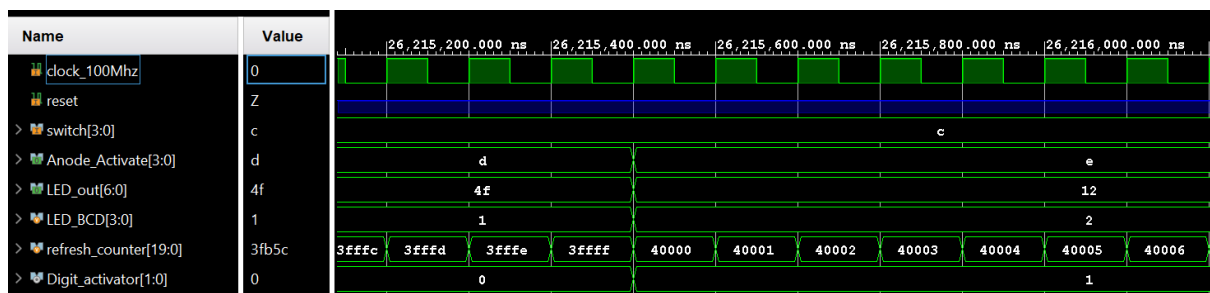


Fig. 7.3: Simulation results of example 7.3

IO Pin Assignment:

Switch[3:0]		Anode_Activate [3:0]		LED_out [6:0]			
Bit 3	W17	Bit 3: Display 1	W4	Bit 6: Seg a	W7	Bit 2: Seg e	U5
Bit 2	W16	Bit 2: Display 2	V4	Bit 5: Seg b	W6	Bit 1: Seg f	V5
Bit 1	V16	Bit 1: Display 3	U4	Bit 4: Seg c	U8	Bit 0: Seg g	U7
Bit 0	V17	Bit 0: Display 4	U2	Bit 3: Seg d	V8		
Reset: T17				Clock: W5			

Hardware Results:

Input: switch[3:0]

SW 3	SW 2	SW 1	SW 0
ON	ON	OFF	OFF

Output:



EXAMPLE 3.4: Write a Verilog code to perform the 4-bit BCD addition and display the results on the seven-segment display of the Basys 3 FPGA kit.

Solution:

BCD inputs (Input1+Input2+Carry)	BCD sum	Binary sum
0000+0101+0	Carry=0, sum=0101	Carry=0, sum=0101
0001+0101+0	Carry=0, sum=0110	Carry=0, sum=0110
0010+0101+0	Carry=0, sum=0111	Carry=0, sum=0111
0011+0101+0	Carry=0, sum=1101	Carry=0, sum=1000
0100+0101+0	Carry=0, sum=1001	Carry=0, sum=1001
0101+0101+0	Carry=1, sum=0000	Carry=0, sum=1010
0110+0101+0	Carry=1, sum=0001	Carry=0, sum=1011
0111+0101+0	Carry=1, sum=0010	Carry=0, sum=1100
1000+0101+0	Carry=1, sum=0011	Carry=0, sum=1101
1001+0101+0	Carry=1, sum=0100	Carry=0, sum=1110

On the 4-digit segment display of the Basys 3 kit, the binary sum is programmed to display on the leftmost two digits, and the BCD sum to be displayed on the rightmost two digits.

Verilog Code:

```
module BCD_Addition(  
    input clock_100Mhz, // 100 Mhz clock source on Basys 3 FPGA  
    input reset, // reset  
    input [3:0] a,b, // two BCD inputs  
    input carry_in, // Initial carry  
    output reg [3:0] Anode_Activate,  
                                     // anode signals of the 7-segment LED display  
    output reg [6:0] LED_out // cathode patterns of the 7-segment LED display  
);
```

```

reg [3:0] sum;
reg carry;
reg bin_carry;
reg [3:0] bin_sum;
reg [3:0] LED_BCD;
reg [19:0] refresh_counter;
wire [1:0] Digit_activator;

always @(a,b,carry_in)
begin
    {bin_carry, bin_sum} = a+b+carry_in; //add all the inputs
    if(bin_sum > 9)
    begin
        carry = 1; //set the carry output
        sum = bin_sum+6; //add 6, if result is more than 9.
    end
    else
    begin
        carry = 0;
        sum = bin_sum[3:0];
    end
end

end

always @(posedge clock_100Mhz or posedge reset)
begin
    if(reset==1)
        refresh_counter <= 0;
    else
        refresh_counter <= refresh_counter + 1;
end

assign Digit_activator = refresh_counter[19:18];

always @(*)
begin
    case(Digit_activator)
    2'b00: begin
        Anode_Activate = 4'b1110;
        LED_BCD = sum;
    end
    2'b01: begin
        Anode_Activate = 4'b1101;
        LED_BCD = {3'b000,carry};
    end
end

```

```

        2'b10: begin
            Anode_Activate = 4'b1011;
            LED_BCD = bin_sum;
        end
        2'b11: begin
            Anode_Activate = 4'b0111;
            LED_BCD = {3'b000,bin_carry};
        end
    endcase
end

```

// Cathode patterns of the 7-segment LED display

```

always @(*)
begin
    case(LED_BCD)
        4'b0000: LED_out = 7'b0000001; // "0"
        4'b0001: LED_out = 7'b1001111; // "1"
        4'b0010: LED_out = 7'b0010010; // "2"
        4'b0011: LED_out = 7'b0000110; // "3"
        4'b0100: LED_out = 7'b1001100; // "4"
        4'b0101: LED_out = 7'b0100100; // "5"
        4'b0110: LED_out = 7'b0100000; // "6"
        4'b0111: LED_out = 7'b0001111; // "7"
        4'b1000: LED_out = 7'b0000000; // "8"
        4'b1001: LED_out = 7'b0000100; // "9"
        4'b1010: LED_out = 7'b0001000; // "A"
        4'b1011: LED_out = 7'b1100000; // "b"
        4'b1100: LED_out = 7'b0110001; // "c"
        4'b1101: LED_out = 7'b1000010; // "d"
        4'b1110: LED_out = 7'b0110000; // "E"
        4'b1111: LED_out = 7'b0111000; // "F"
        default: LED_out = 7'b1111111; // "0"
    endcase
end
endmodule

```

Simulation Results:

Input: a[3:0] = 1000, b[3:0]=0101, carry_in=0, reset = 1→0, clock=100MHz

Output:

Clock_pulses	Digit_activator	LED_BCD	LED_out (7-segment code)
at 1 st pulse	0 (1 st 7-seg display)	0	0000001
at (1x2 ¹⁸) th pulse	1 (2 nd 7-seg display)	d	1000010

at $(2 \times 2^{18})^{\text{th}}$ pulse	2 (3^{rd} 7-seg display)	1	1001111
at $(3 \times 2^{18})^{\text{th}}$ pulse	3 (4^{th} 7-seg display)	3	0000110

The above sequence keeps repeating at an interval of 2^{18} clock pulses

 


Fig. 7.4: Simulation results of example 7.4

IO Pin Assignment:

a[3:0]	B[3:0]	Anode_Activate [3:0]		LED_out [6:0]			
W17	W13	Bit 3: Display 1	W4	Bit 6: Seg a	W7	Bit 2: Seg e	U5
W16	W14	Bit 2: Display 2	V4	Bit 5: Seg b	W6	Bit 1: Seg f	V5
V16	V15	Bit 1: Display 3	U4	Bit 4: Seg c	U8	Bit 0: Seg g	U7
V17	W15	Bit 0: Display 4	U2	Bit 3: Seg d	V8		
Reset: T17		carry_in: R2		Clock: W5			

Hardware Results:

Input:

carry_in	b[3:0]				a[3:0]			
SW 15	SW 7	SW 6	SW 5	SW 4	SW 3	SW 2	SW 1	SW 0
OFF	OFF	ON	OFF	ON	ON	OFF	OFF	OFF

Output:




EXERCISE PROBLEMS:

1. Write the structural Verilog code to realize a 3x1 multiplexer using 2x1 multiplexers, synthesize, and implement it through the onboard user switches and LEDs of the Basys 3 FPGA kit.
2. Write a Verilog code to display the push button's status on the seven-segment display of the Basys 3 kit as follows:

Pressed Push Button	Character to be displayed on the seven segment display
BTNR	P
BTNU	U
BTNL	L
BTND	d
BTNC	C

 - Write a data flow Verilog code to create a 4-bit ripple carry adder, synthesize, and implement it on Basys 3 hardware.
- Design and implement a popular IC, 74138, functionality using dataflow modeling of Verilog. The IC symbol and truth table are given below. Verify the functionality on Basys 3 hardware.



- Design a comparator that compares two 2-bit numbers (A and B) and assert outputs indicating whether the decimal equivalent of word A is less than, greater than, or equal to that of word B. Realize it on Basys 3 hardware.